

Design

 


Figure 1: CMOS Inverter Schematic

Euler's Path

PMOS	NMOS
COMMON PATH: A	

 


Figure 2: Inverter Stick Diagram

 


Figure3: 2-input NAND Gate Schematic

Euler's Path

PMOS	NMOS
COMMON PATH: A - B	



 


Figure 4: Stick Diagram for 2-input NAND Gate Schematic

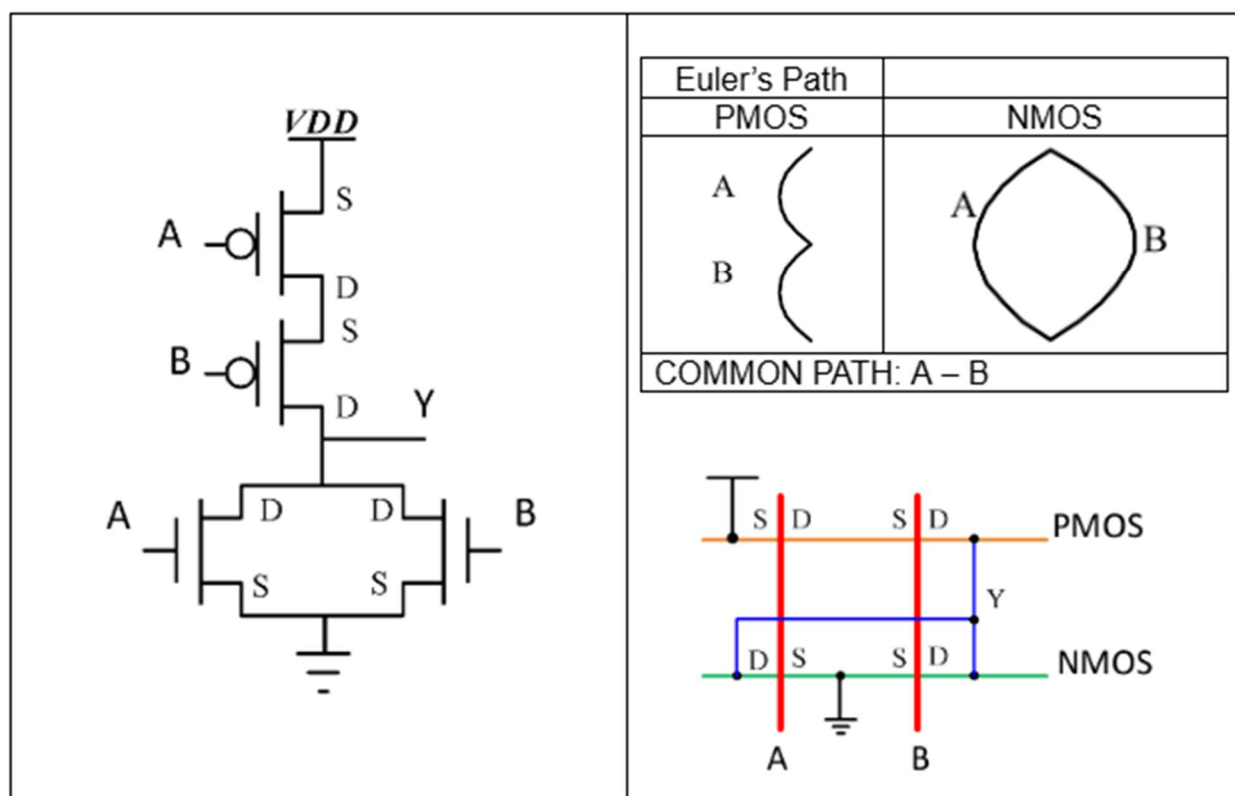

Half Adder

 


COMMON PATH: $\overline{B} - \overline{A}$	
Figure 4: Stick Diagram for SUM Logic	Figure 5: Stick Diagram for CARRY Logic
Euler's Path for CARRY Logic	
PMOS	NMOS

Design

1) Using Logic Gates

$$Y = A \cdot \bar{S} + B \cdot S$$

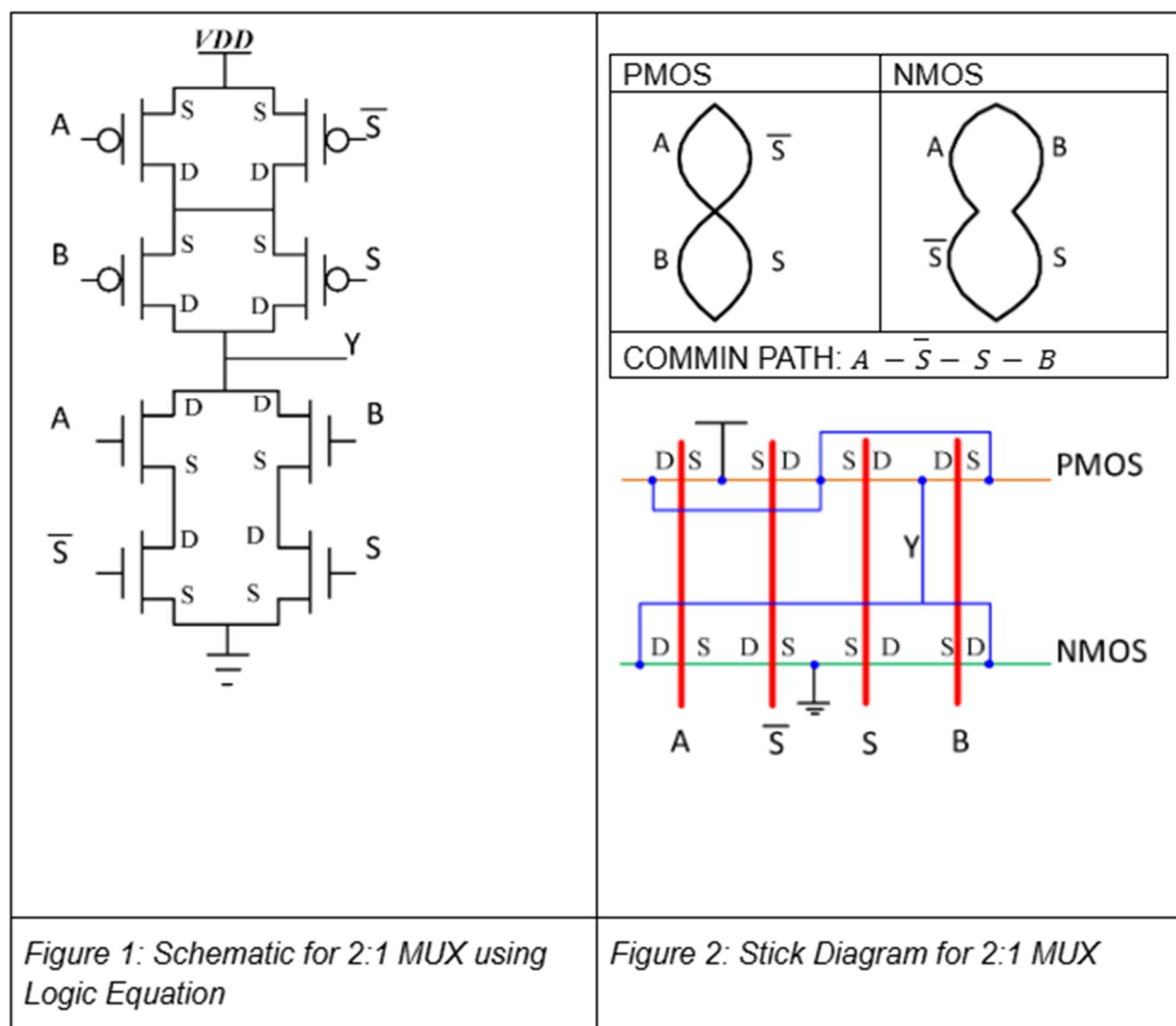

2) Using Transmission Gates

 


Figure 3 Schematic for 2:1 MUX using Transmission Gates

 


Figure 4 Alternative Form of Figure 18

 


Figure 5 Stick Diagram for 2: 1 MUX