Instructions

Check

Reset

Add to
Table

Voltmeter

Ammeter

Speedo Meter　1015

220 V

1 A

Field Resistance

D.C Motor

Front View of
D.C Motor

Armature
Resistance

Plot Graph

OBSERVATION TABLE

S.No.	Current (A)	Speed (RPM)
1	0.1	2500
2	0.2	2340
3	0.3	2100
4	0.4	1930
5	0.5	1700
6	0.6	1575
7	0.7	1480
8	0.8	1400
9	0.9	1270
10	1	1015

Speed (RPM) vs Current (A)

Speed (RPM)

Current (A)

Print

Copyright © 2019 Virtual Labs, IIT Roorkee